


Tristate Outputs

all 3 are valid

logic 0, logic 1, high impedance (Hi-Z)


neither 1 or 0, acts like an open circuit (when both transistors are off)

when a device is enabled, O/P is logic 0 or 1


when disabled, O/P is Hi-Z

eg. tristate buffer, tristate inverter


Tristate Inverter

 

Tristate Buffer

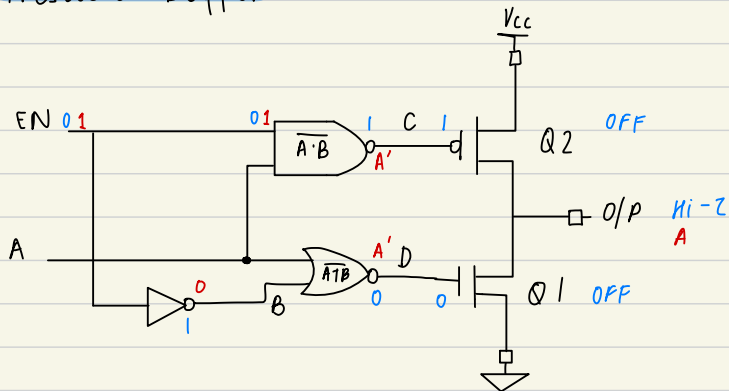


EN	A	B	C	D	Q1	Q2	OUT
L	L	H	H	L	OFF	OFF	Hi-Z
L	H	H	H	L	OFF	OFF	Hi-Z
H	L	L	H	H	ON	OFF	L
H	H	L	L	L	OFF	ON	H

 

Advantages of logic devices with tristate outputs


- 2/t o/p can be connected together BUT only 1 can be enabled
- else bus contention takes place which results in a wrong o/p
- when o/p's are connected together, they share the same data bus
- nontristate output is essentially enabled and cannot be connected to a tristate output

Open-collector / drain output

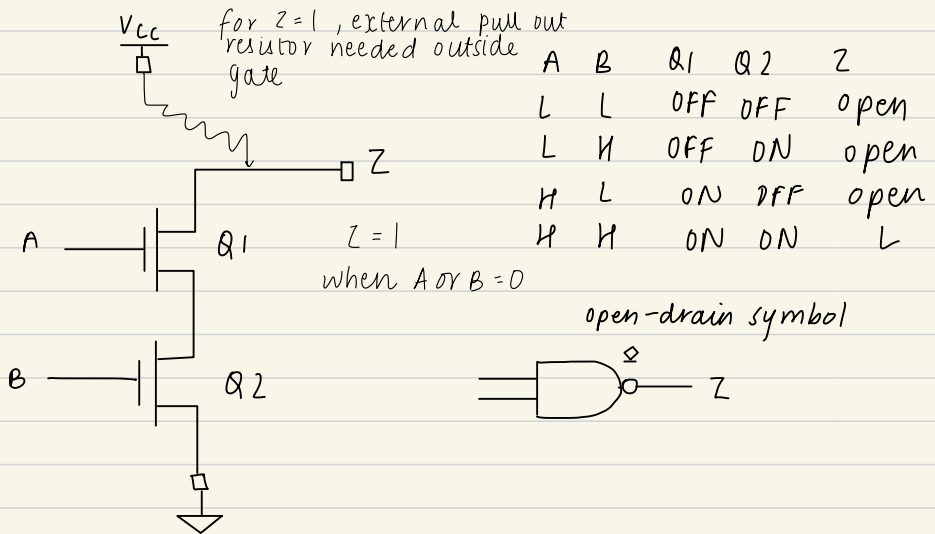

open-drain can drive LED

↑ can be tied together
↑
≡ to a AND gate

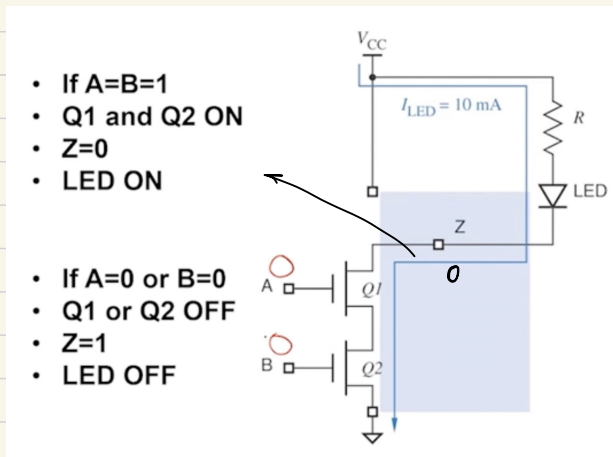


L11 practice problems

1. Two different logic circuits have the characteristics shown below.
 - (a) Which circuit has better DC noise margin?
 - (b) Which circuit has better DC fan-out?
 - (c) Which circuit can operate at a higher frequency?
 - (d) Are the two circuits able to drive each other?

	Circuit A	Circuit B
V_{CC} (V)	5	5
$V_{IH(min)}$ (V)	1.6	1.8
$V_{IL(max)}$ (V)	0.9	0.7
$V_{OH(min)}$ (V)	2.2	2.5
$V_{OL(max)}$ (V)	0.4	0.3
$I_{IH(max)}$ (mA)	1.0	1.5
$I_{IL(max)}$ (mA)	1.0	1.5
$I_{OH(max)}$ (mA)	20	27
$I_{OL(max)}$ (mA)	25	30
t_{PLH} (ns)	10	18
t_{PHL} (ns)	8	14
PD (mW)	16	10

(Adapted from Tocci, Widmer and Moss, ed. 10)

 2. The figure below shows how two tristate buffers can be used to construct a bidirectional transceiver that allows digital data to be transmitted from A to B, or from B to A. Describe the circuit operation.
(Tocci, Widmer & Moss, ed. 10)



3. Describe the operation and hence obtain the Boolean expression for this CMOS circuit.
(Wakerly Ex. 3.59)

