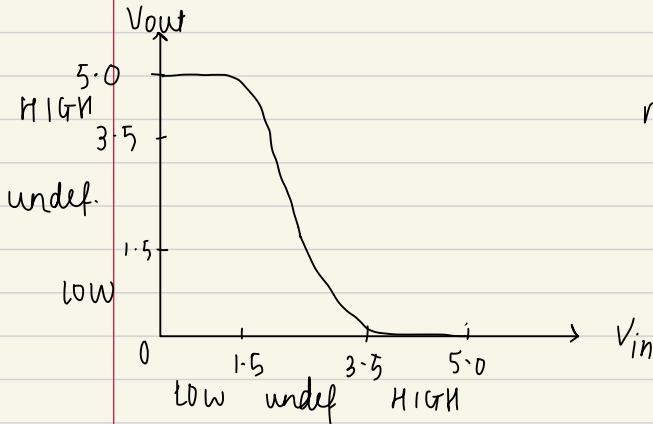



Digital Circuits characteristics

- I/O of CMOS inverter (typically)



not guaranteed.

Char 1

Voltage parameters

$V_{OH}(\min)$ - minimum O/P voltage produced for logic 1

$V_{IH}(\min)$ - minimum I/P voltage to be recognised as logic 1

$V_{OL}(\max)$ - max O/P voltage produced for logic 0

$V_{IL}(\max)$ - max I/P voltage to be recognised as logic 0


CMOS

5.0
3.5 $\leftarrow V_{IH}, V_{OH}$
1.5 $\leftarrow V_{IL}, V_{OL}$
0

$V_{OH} \geq V_{IH}$
 $V_{OL} \leq V_{IL}$

Char 2

Noise margin

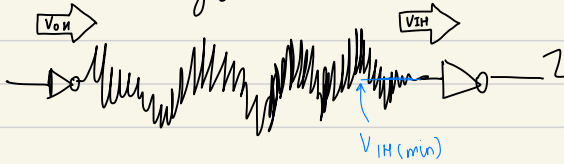

- high-state DC noise margin = $V_{OH(min)} - V_{IH(min)}$
- higher the noise tolerance, the better
- low-state DC noise margin: $V_{IL(max)} - V_{OL(max)}$
- higher power supply \Rightarrow better noise margin
- overall noise margin = $\min \left(\begin{matrix} \text{high-state} & , & \text{low-state} \\ V_{OH} - V_{IH} & & V_{IL} - V_{OL} \end{matrix} \right)$

Char 3

Current Parameters

- $I_{IH} \text{ (max)}$: max current in the input at logic 1.
- $I_{IL} \text{ (max)}$: max current that flows into input at logic 0
- $I_{OH} \text{ (max)}$ = max current flowing from output at logic 1
- $I_{OL} \text{ (max)}$ = max current flowing from output at logic 0
- In CMOS, current is very small, esp at I/P (1 μA) and for O/P there's a range (0.02 - 24 mA) depending on the family

Char 4

FAN-OUT

- specifies the number of standard loads/gates an output can drive
- more gates \Rightarrow more current you need to have
 \therefore current parameter \propto fan-out
- more loads can reduce noise margin (bad) and may increase switching speed
- high state fan-out = I_{OH}/I_{IH}
low state fan-out = I_{OL}/I_{IL}

char 5

SPEED

- switching speed measures how much time it takes for the output to switch b/w logic 0 and 1
- Shorter, the better

char 6

Power Dissipation

- power consumed by the gate or device
- in CMOS, most power is consumed when it switches between 0 and 1 (dynamic power dissipation)

$$P = C V^2 f \quad (\text{gets heated})$$

↑ ↑ ↖ switching frequency
constant power supply voltage

- static power dissipation (when its at logic 0, logic 1)
is very small.

char 7

Propagation Delay

avg transition delay time for signal to propagate from input to output


typically in nanoseconds

t_{PD} or (t_{PHL} & t_{PLH})

$H \rightarrow L$

$L \rightarrow H$

change in O/P

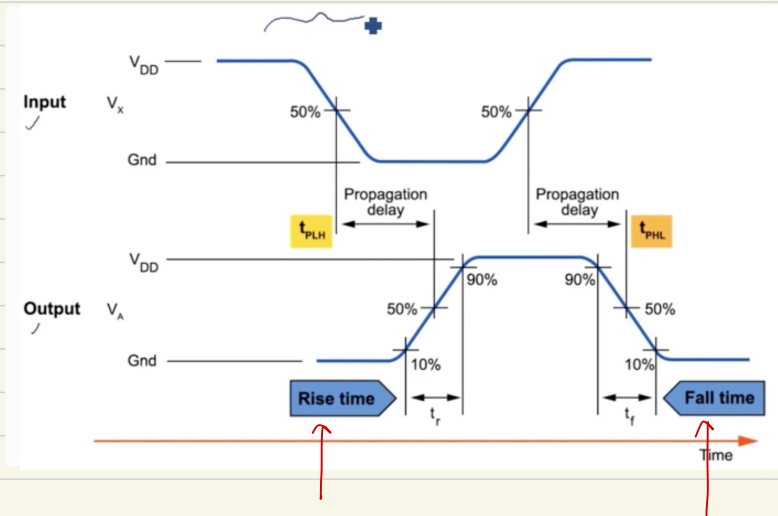

time taken for signal to go from 0-1 (logic)

should be as short as possible