


---

decoder, mux,  
encoder, timing  
diagram

---




## Combinational Circuits

↳ ex. decoder, multiplexer etc.


task 1

$$w = pks'$$

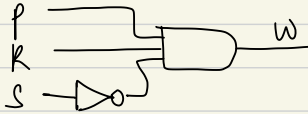

↑  
o/p doesn't depend on previous input values

## seven segment decoder

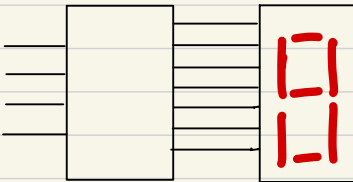

takes 4 bit inputs and shows its hexa counterpart


· n inputs, max  $2^n$  outputs

## decoder

- binary input and gives a one-hot output
- n inputs, def.  $2^n$  outputs



2-4

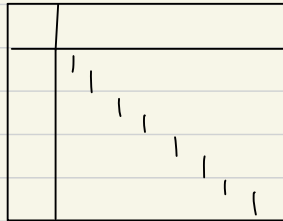

3-8

internal design


- and gates for each output
- enable e (active high)

example 6 bit input  $\rightarrow$  1 bit output displays 1 bulb at a time  
and there's 60 in total  
counts from 59 to 0

$\rightarrow$  6-bit =  $2^6 = 64$   $\therefore$  enable  $e = 1$  from 0 to 59  
 $e = 0$  from 60 to 64
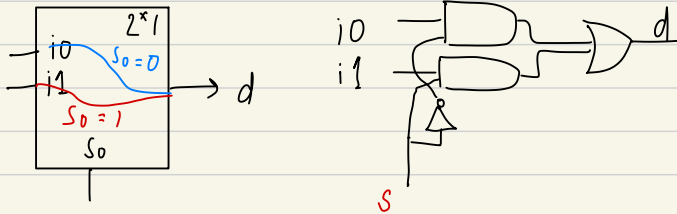
### multiplexer

- multiple inputs, single output, selection input
- at a time, only one input is connected to the output




$n \times 1$  mux:

$n$  inputs,  $\log_2 n$  selection inputs, 1 output

+91 9490118203


multi-bit inputs

4 bit  $2 \times 1$  mux

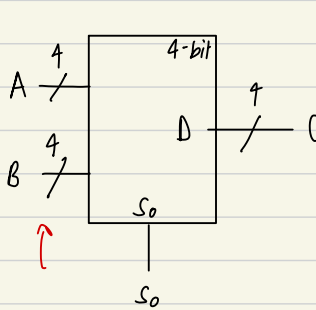


notation  
4 bit bus


$a_3$   
 $a_2$   
 $a_1$   
 $a_0$

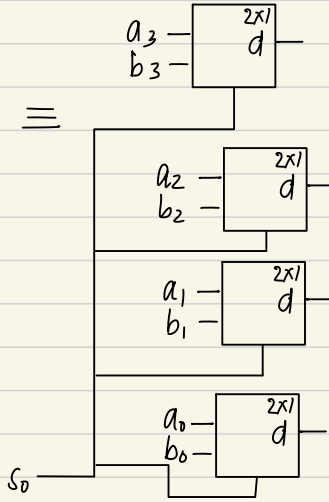

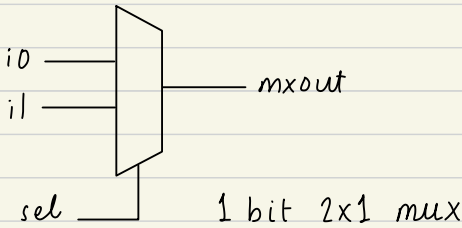at a time,  
only A  
or B  
is displayed




1 bit  $2 \times 1$  mux

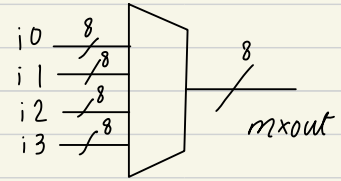

8 bit  $4 \times 1$  mux

A	B	f
0	0	
0	1	
1	0	B
1	1	B

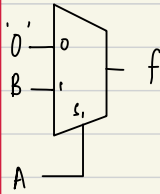

A	f
0	0
1	B


2-input AND gate

(1)  
(6)


A	B	C	F
0	0	1	1
1	1	0	1
0	1		
	0		
1	1		

} → 0

∴ NOT

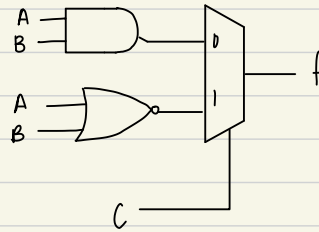

A	B	C	F
0	0	1	1
1	1	0	1

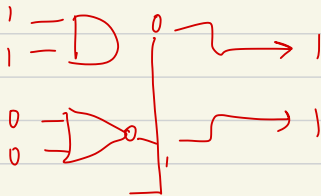

## timing diagrams

- show behavior of circuit with progression of time
- input values are changed and the resultant outputs shown
- can show any combo of input values