

---

assignment

vectors

number literals




# Verilog Assignments

allows for description of a circuit's structure

instantiating gate primitive : and (y, a, b);

continuous assignment : assign y = a & b use of boolean statements  
allows for description of a circuit's function

~	NOT	} bitwise
&	AND	
	OR	
^	XOR	
~&	NAND	
~	NOR	

 

assign out = (a & b) ~| (c & d);

~ & | ^ ~^ ← l to R precedence

eg2. full adder.

$$S = A \oplus B \oplus C_{in} \quad C = AB + BC + AC = AB + C_{in}(A+B)$$

```
module full-adder (input a, b, cin,
                  output S, c);
```

happen concurrently

∴ order does not matter


```
    assign S = a ^ b ^ cin;
    assign c = (a & b) | cin & (a | b);
```

```
endmodule
```

conditional assignment  $\xrightarrow{\hspace{1cm}}$  basically an if statement

assign  $y = \text{sel} ? x_1 : x_0 ;$  // a multiplexer

$\therefore$  conditional  $\equiv$  mux

 

combinational arithmetic

$+, -, *, /$  (div is not usually synthesizable)  
 $<, <=, >, >=, ==, !=$



comparisons give true (1) or false (0)


eg3. assign sum = a + b;  
assign diff = curr - prev;  
assign max = (a > b) ? a : b;

# Vectors in Verilog

multi-bit inputs

MSB ↘ ↙ LSB  
wire [31:0] databus;

range of the wire : 32 bits

 


eg 4 module add16 (input [15:0] a, b,  
output [15:0] sum,  
output cout);

2 16 bit inputs + 0/p  
1 1 bit output

endmodule

 eg 5 module adder (  
input cin,  
input [31:0] A, B,  
output cout,  
output [31:0] sum);



multibit wires must be declared → wire [32:0] w1;

assign w1 = A + B + cin;  
assign sum = w1[31:0];  
assign cout = w1[32];

← assigning the msb of a vector to another

endmodule

assign cout = w1[32:10]; also valid  
assign A[15] = B[10]; also valid

careful: multi-bit 1 bit

↓ ↓

assign x[2:0] = y[1] ≡ 

x2	0
x1	0
x0	< y[1] >

 } verilog adds 0 to cover gap

concatenation

wire [3:0] a, b;

wire [7:0] y;

:

assign y = {a, b};



y[7] = a[3]

⋮

y[4] = a[0]

y[3] = b[3]

y[0] = b[0]

concatenation operators

replication

assign c = { {4{a[3]}}, a[3:0] };   
(Note: In the original image, the braces and indices in this line are underlined in blue)

a = 1010 ⇒ c = 11111010

## Number Literals

- assigning values

assign s = 1 ;      dec? hexa? oct?  
                                 how many bits?

- <size> : in bits  
<radix> : b for binary, 0... , h... , d...  
<value> : number w/ optional underscores for readability

assign s = <size>'<radix><value> ;  
assign s = 4'b0001 ;

- if a literal is assigned to a larger signal, it is zero padded at the MSB  
and if the opposite is done, it is truncated at the MSB

eg 5. assign b = { a[3:0] , 4'b0000 } ;

$$a = 1010_2 \quad \Rightarrow \quad b = 10100000$$

## Parameter

- constant that is local to a module

→ can be declared in the module header

```
module some_mod #(parameter SIZE = 8)
  [ input [SIZE-1:0] X, Y,
    output [SIZE-1:0] Z ];
```

*syntax* *keyword* *constant's name*

can have multiple

⇒ X, Y [7,0] and so on

when instantiating

```
some_mod #( .SIZE(value) ) U1 ( .X(a), .Y(b), .Z(c) );
```

eg 6

```
module adder #(parameter SIZE = 32) (
  input Cin,
  input [SIZE-1:0] A, B,
  output Cout,
  output [SIZE-1:0] sum);
```

```
assign {Cout, sum} = A + B + Cin;
```

endmodule

*msb* *[31:0]* *operator to generate sum*

