

---

---

---

---

---




- has a certain number of states
- a plan to transition from one state to another

## Finite State Machines

- very efficient model to describe the behavior of our circuits.
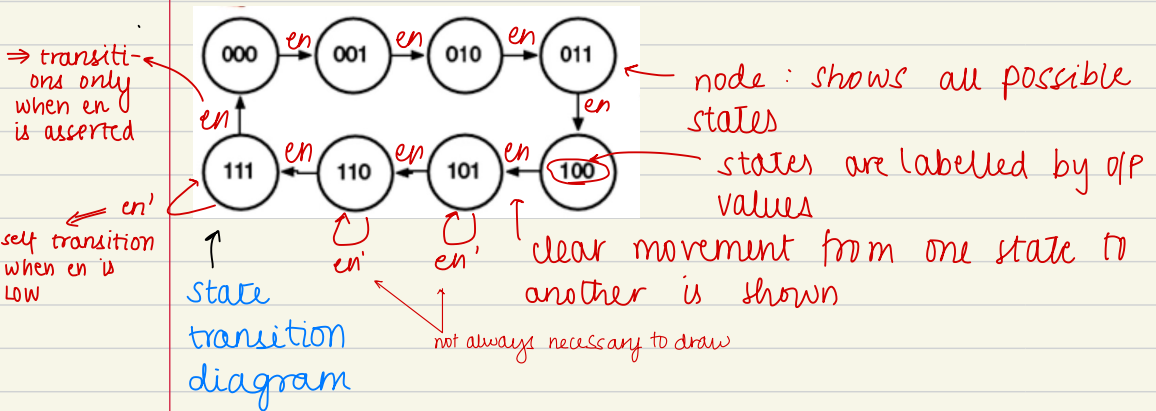
### Sequence and State of Counters

- at a pt in time it has state A
- at the transition point, it changes to the next state corresponding with the next largest output




- still a sequential circuit  $\Rightarrow$  change of state can only occur at the rising edge of a clock

## Up-Down Counters

count up :  $dn = \text{LOW}$   
down :  $dn = \text{HIGH}$

all while :  $en = \text{HIGH}$

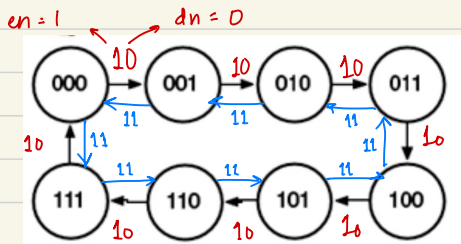

inputs :  $en, dn$

self transitions (00, 01)  
can be excluded from  
the diagram

Back to FSM

general object that can  
execute an abstract language


it's a system using a finite number of states and associated transitions

in synchronous design, an FSM is in one state for the duration of each clock cycle

at every rising clock edge, the FSM may transition to another state

↓  
depends on input values at the rising edge


always on machine

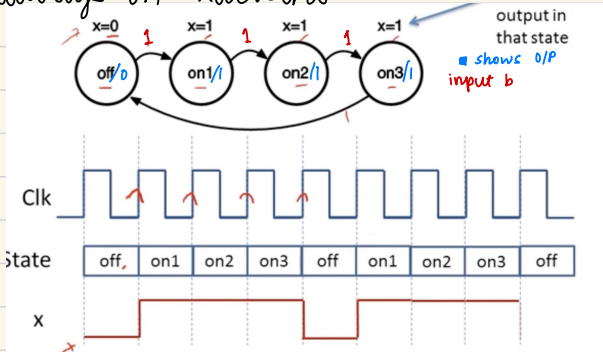

state transition table

Current State	Next State		Output
	b=0	b=1	
off	off	on1	0
on1	on2	on2	1
on2	on3	on3	1
on3	off	off	1

task 1  
q1


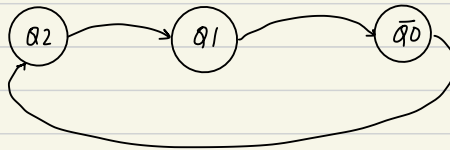


← x


Q2Q1Q0 is the O/P

at power up/reset  $Q2Q1Q0 \rightarrow 000 \Rightarrow (\bar{Q0} = 1) \rightarrow 100 \rightarrow 110 \rightarrow 111$   
 $\uparrow$   
 $000 \leftarrow 001 \leftarrow 011 \leftarrow$


Q2

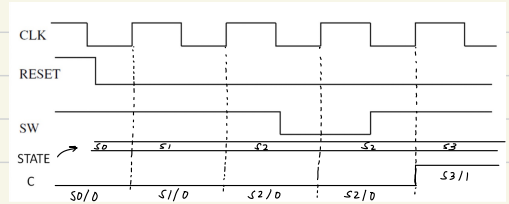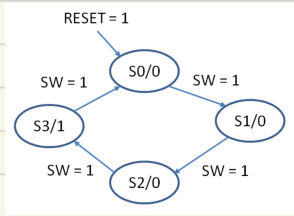

FSM for a vending machine

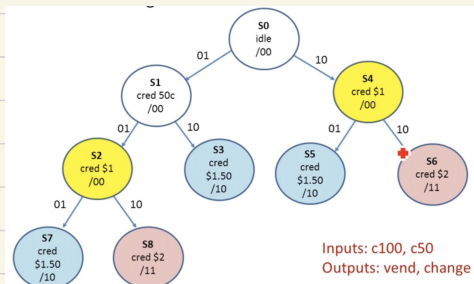


simp-  
lifted

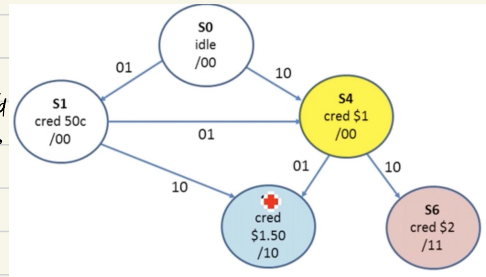

task 2

→ coin , → push

output : light

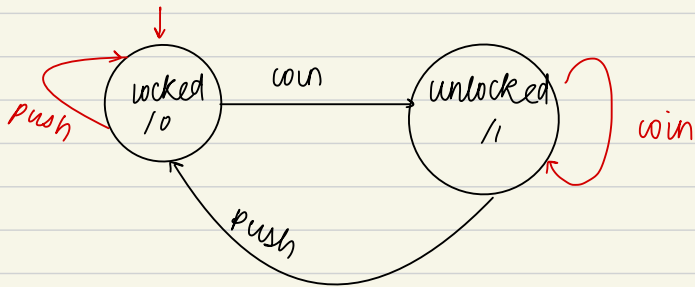

## Moore vs Mealy

- Moore machines : outputs depend only on state  
ie. in state  $x$ , output is always  $f$
- Mealy machines : output depends on the state and  
current values of inputs  
ie. if inputs change mid-state, then output also  
change