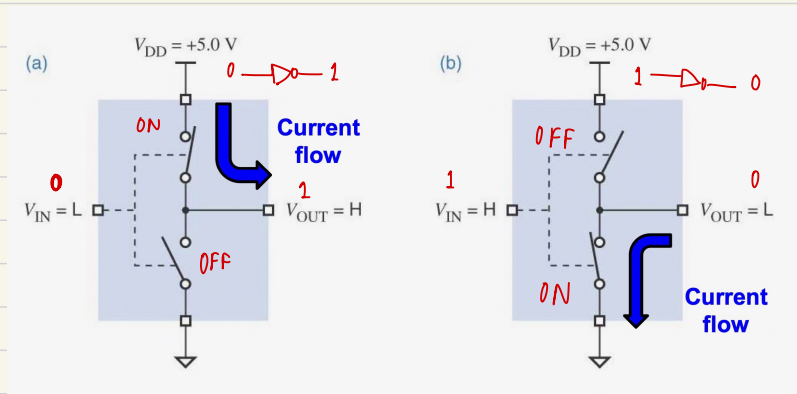



a good logic circuit diagram



- all indicated
- pin numbers, IC numbers, component values, signal names and power supply voltages clearly indicated
 - bubble to bubble design
 - active levels

back to transistors as a switch



BJT INVERTER



TTL INVERTER



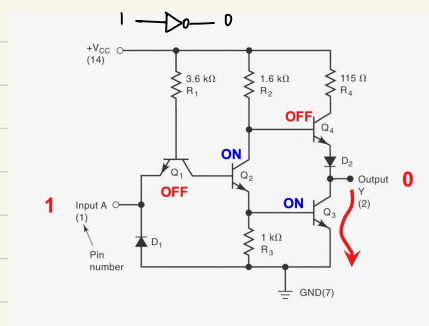
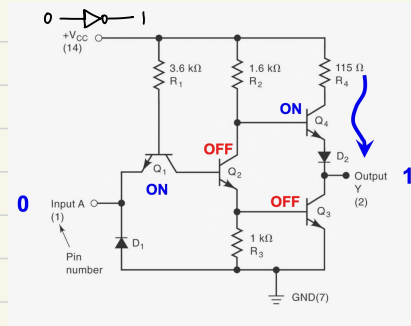


CMOS INVERTER

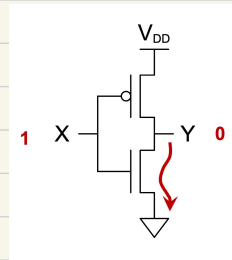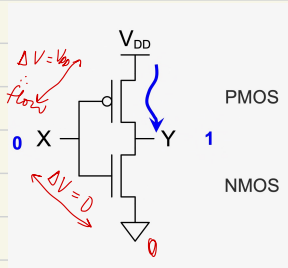

CMOS LOGIC CIRCUITS

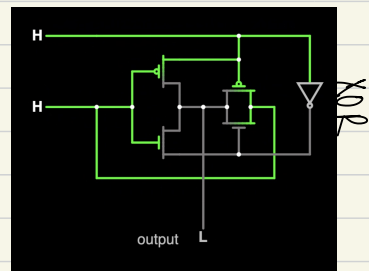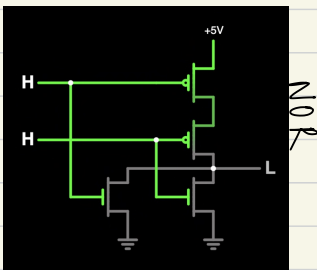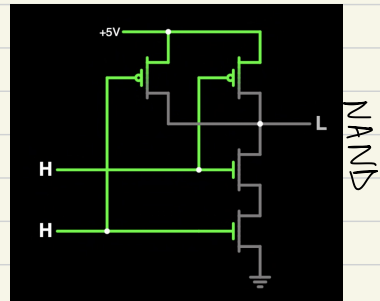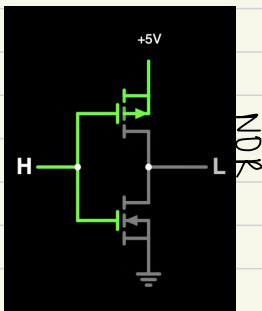- series : all must work
- parallel : at least one must work



L10 practice problems

CMOS Logic

Determine the truth tables for the following CMOS logic circuits.

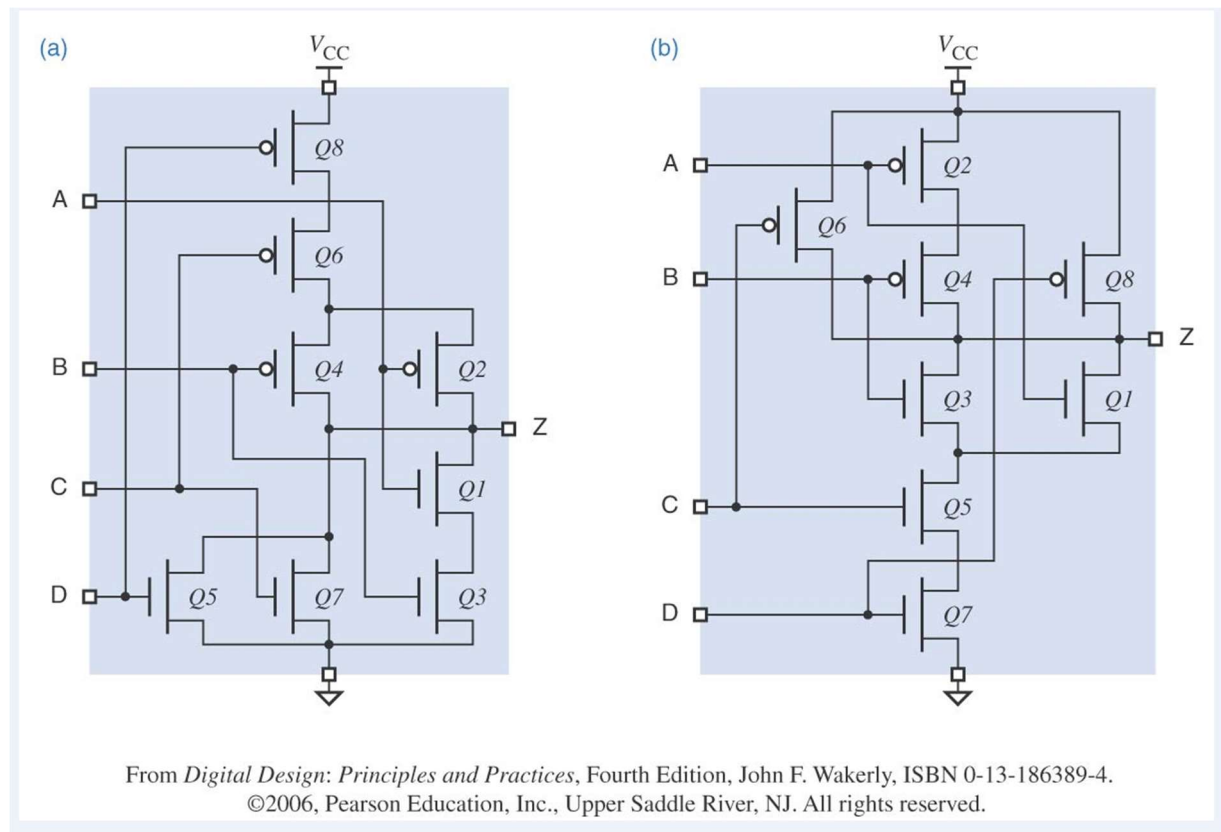


Fig. X3.11

Hint:

From the circuit diagram

Step 1: identify the inputs (e.g. A, B, C, D)

Step 2: identify the pair of transistors directly controlled by each input (e.g. input A controls Q1 and Q2)

Step 3: identify all the possible current paths (series as well as parallel) from Vcc to output so as to make output = 1.

For each possible path, identify the correct input values, and fill up the corresponding rows in the truth table with output=1

Step 4: identify all the possible current paths (series as well as parallel) from output to GND so as to make output = 0.

For each possible path, identify the correct input values, and fill up the corresponding rows in the truth table with output=0

					(0) A : Q8 , Q2 , $\overline{Q1}$
					(0) B : Q4 , $\overline{Q3}$
					(0) C : Q6 , $\overline{Q7}$
					(0) D : $\overline{Q5}$, Q8

(0) D : $\overline{Q5}$, Q8