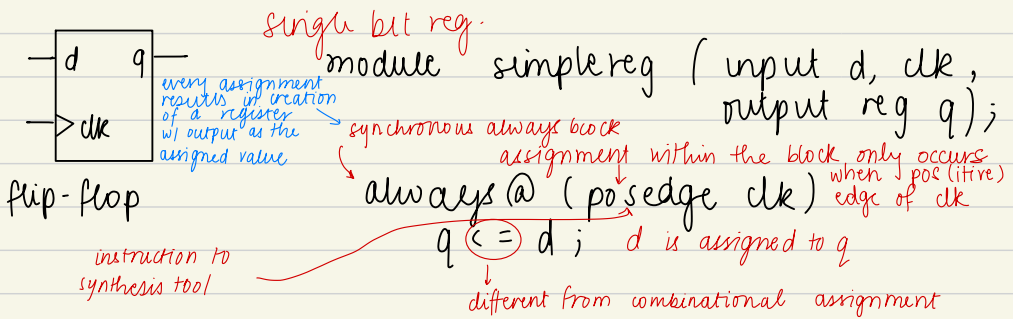



Sequential Verilog


- small blocks can be integrated into larger designs using instantiation
- we usually describe synchronous circuits (edge-triggered components)
- the synthesis tool will generally convert designs to D-type flip-flop / registers



at the rising edge of the clock, input is passed to output



endmodule

 

```

module multireg (input [7:0] d, input
                  clk, output reg [7:0] q);
    always @ (posedge clk)
        q <= d;
    
```

falling-edge trigger:
always @ (negedge clk)


endmodule

resetting values in a register

asynchronous : whenever reset input is asserted, the contents are set to the reset value

synchronous : at rising edge, if reset is asserted, then contents are set to the reset value

↑
preferred

 

module simplerreg (input [7:0] d,
input clk, rst,
output reg [7:0] q);

always @ (posedge clk)

begin

if (!rst)

q <= 8'b0000-0000;

else

q <= d;


end

endmodule

sometimes
rst is
active
low

or posedge rst

recommended use a synchronous reset

 

- asynchronous reset :

```
module simplereg (input [7:0] d,  
                  input clk, rst,  
                  output reg [7:0] q);  
  always@(posedge clk or posedge rst)  
  begin  
    if (!rst) // if active low  
      q <= 8'b0000-0000;  
    else  
      q <= d;  
  end  
endmodule
```

- multiple registers

```
module multireg (input [7:0] a, b, c,  
                 input clk, rst,  
                 output reg [7:0] q, r, s);  
    always @(posedge clk)  
    begin  
        if (!rst)  
            begin  
                q <= 8'b0000-0000;  
                r <= 8'b0000-0000;  
                s <= 8'b0000-0000;  
            end  
        else begin  
            q <= a;  
            r <= b;  
            s <= c;  
        end  
    end  
endmodule
```

reset and clk may be
left out in the
diagrams, but they
should be there

Assignment

\leq : non-blocking assignment

combinational: $=$, order matters

synchronous: \leq , order doesn't matter


↳ always for always@*

↳ always for always@
(posedge clk)

↳ look into this

but timing matters
it is one after the other

 results in a register:
eg. $a \leq b + c$;



Counters



binary counters

- increasing output value in each cycle

2 bit . $\left. \begin{array}{c} 00 \\ 01 \\ 10 \\ 11 \end{array} \right\}$ and repeat

counters can count down also

- synchronous counters

  

combinational increment

module simplecnt (input clk, rst, output reg [3:0] q);
always @ (posedge clk)
begin

if (rst)
q <= 4'b0000

else
q <= q + 1'b1;


end
endmodule

old value

down

else
if (down)
q <= q - 1'b1;
else
q <= q + 1'b1;

input custom value into counter

 

```
module simplecnt (input clk, rst,  
                  input down, load,  
                  input [3:0] cnt_in,  
                  output reg [3:0] q);
```

```
always @(posedge clk)
```

```
begin
```

```
  if (rst)
```

```
    q <= 4'b0000;
```

```
  else
```

```
    if (load)
```

```
      q <= cnt_in;
```

```
    else
```

```
      if (down)
```

```
        q <= q - 1'b1;
```

```
        q <= q + 1'b1;
```

```
  end
```

```
endmodule
```

don't mix
rst is not part of the body
of the counter while
load is