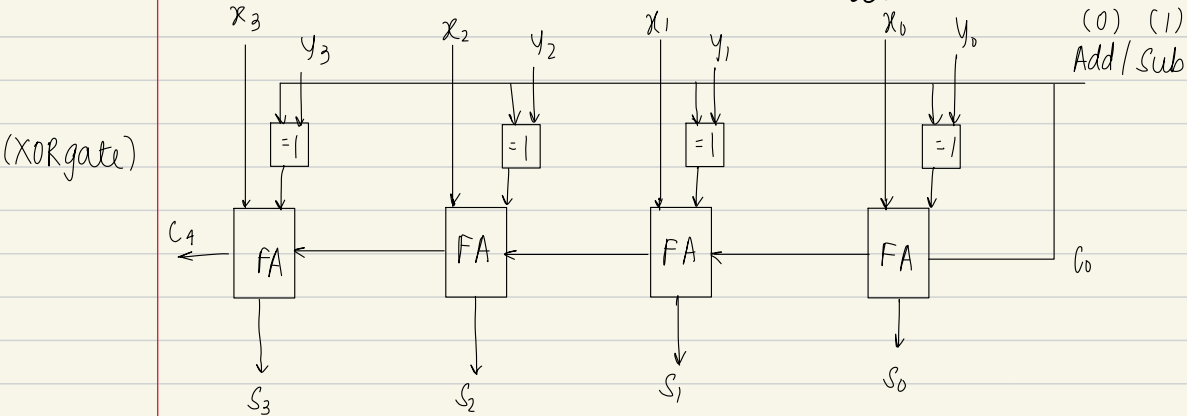



Combined adder+subtractor



- so the add/sub input helps convert to 2's comp if needed so lets see.

add $1/P=0$

$$\begin{array}{r}
 y = 001101 \\
 \downarrow \downarrow \downarrow \downarrow \downarrow \\
 + 001101
 \end{array}$$

sub $1/P=1$

$$\begin{array}{r}
 y = 1001110 \\
 \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \\
 0110001 \\
 + 1 \\
 \hline
 0110010
 \end{array}$$

2's complement of y

now XOR is odd no of 1s and incase of 2 inputs, diff $1/P \Rightarrow 1$, same input $\Rightarrow 0$ so when one input is 0, the output is equal to the other input and when one input = 1, the output is the opposite of the other input

AND this add/sub $1/P$ also is the first carry. So incase of subtraction, the XOR gates take the 1's complement and this carry bit is the '1' that has to added to convert to 2's complement

imp, this sign det the add/sub I/P value

$$2 + (-4)$$

ex

$$X = 0010$$

$$0010$$

$$Y = 1100$$

$$1100$$

$$Y_{\text{into FA}} = 1100$$

$$C_0 = 0$$

$$S \rightarrow 1110$$

$$C_4 = 0$$

$$-2 - (-4)$$

$$X = 1110$$

$$111$$

$$1110$$

$$Y = 1100$$

$$0011$$

$$Y_{\text{into FA}} = 0011$$

$$C_0 = 1$$

$$1$$


$$10010$$

$$C_4 = 1$$

$$\rightarrow 2$$

• 15 vid 2 parallel adder w/ registers

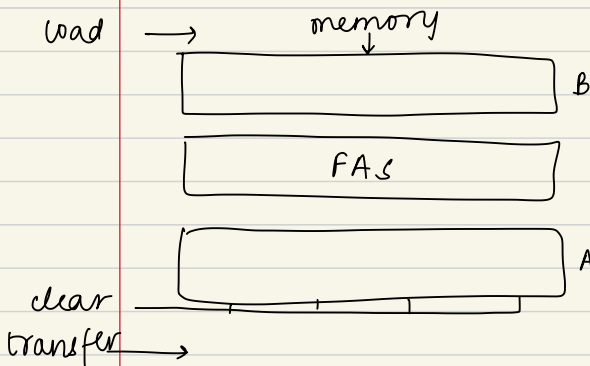• registers are digital memory circuits used to store digital data. N bit registers store N-bits of data



- ① clear A to zero
- ② load X to B from memory
- ③ add 0000 to X and store in A
- ④ load Y to B
- ⑤ add X(A) to Y(B) and store in A

6543210

$$1100110 \rightarrow (64 + 42 + 4 + 2) = 112$$

$$- 1111001 \rightarrow (64 + 32 + 30 + 8 + 1) = 136$$

$$= -19$$

$$-64 + 32 + 1 + 4 + 8$$

$$= -32 + 13$$

$$= -19$$