


Behavioral Modeling

- describes how the circuit behaves, not how it is constructed : **behavioral design**
- logic synthesizers read the description and build the circuit

Combinational Always Block

eg 1

always @ (a, b) ← **sensitivity list** (must contain the names of any signals that will affect the output of the block)

→ begin

x = a & b ;

y = a | b ;

→ end

} → **procedural statements**
order matters
or sequential statements

if there
is more
than 1
statement

- instead of writing out every signal in the sensitivity list, just put a *

always @ *

- don't ever use an assign statement in the always blk
- for a signal inside an always block, keyword **reg** is used outside the block to declare it

eg.

module

reg w1;


always @ *

w1 = a & b ;

assign out = w1 ;

endmodule

- reg is more like a variable while a wire is
- can't assign to reg using an assign statement
- if output is assigned within the always block, then in the module desc it should say:
output reg (name);

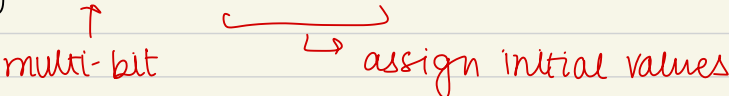- reg [3:0] x = 4'b0000; is valid


- can use if statements (java syntax) in always blocks (nested too)

↑
if there's more than one statement in any of the blocks, a begin...end must be used in that block.

↓
≡ {} in C

↳ in verilog {} = concatenation

- group signals in always blocks only if it makes logical sense

case statements (almost like switch)

eg 2.


```
always @ *
  case (sel)
    2'b00 : y = a;
    2'b01 : y = b;
    2'b10 : begin
              y = c;
              z = d;
            end
    default : y = 4'b0101;
  endcase
```

↑ used in Decoder

decoder is a one-hot output

3-to-8 decoder	module decoder3_8 (output reg [7:0] d_out, input [2:0] i_val);
single statement →	always @ *
	case (i_val)
	3'b000 : d_out = 8'b00000001;
	...
	3'b111 : d_out = 8'b10000000;
	endcase
	endmodule

Implementing a multiplexer

 

```
module mux4 (output reg q,  
             input [3:0] d,  
             input [1:0] sel);
```

```
    always @ *
```

```
    begin
```

```
        case (sel)
```

```
            2'b00 : q = d[0];
```

```
            2'b01 : q = d[1];
```

```
            2'b10 : q = d[2];
```

```
            2'b11 : q = d[3];
```

```
        endcase
```

```
    end
```

```
endmodule
```

unnecessary

```
module Y (output reg q,  
          input [3:0] d,  
          input [1:0] sel);
```

DOUBT

```
    always @ *
```

```
        assign q = d[sel];
```

```
endmodule
```

converts to dec?

But what is an always block?

- acts as an infinite loop
- order matters as it is executed sequentially
- order of placement of always block in the module doesn't really matter