 


 

- state register
 - combinational logic to determine next state
 - logic to compute the output
- FSM \rightarrow circuit requirements



- mapping FSM : m states $\Rightarrow (\log_2 m)$ bits to encode
- ↑
point is to uniquely define each state using minimum number of bits (not necessarily in ascending order, just unique)

■ The transition table:

	Inputs			Outputs		
	s1	s0	b	x	n1	n0
off	0	0	0	0	0	0
	0	0	1	0	0	1
on1	0	1	0	1	1	0
	0	1	1	1	1	0
on2	1	0	0	1	1	1
	1	0	1	1	1	1
on3	1	1	0	1	0	0
	1	1	1	1	0	0




4 states
2 bits

Combinational Logic

Input: $s1, s0, b$


Output: $(n1, n0, x)$

 

inputs	outputs
0 0	0
0 1	1
1 0	1
1 1	1

clearly, $n1$ is XOR
and $n2$ is $b s0' s1' + s1 s0'$

clearly an OR operation
⊕ logic for x

 


```
module pulse3 (input b,  
               input clk, rst,  
               output x);
```

```
    wire n1, n0;  
    reg s1, s0;
```

```
    assign n1 = s1 ^ s0;  
    assign n0 = (~s1 & ~s0 & b) | (s1 & ~s0);  
    assign x = s1 | s0;
```

```
    always @ (posedge clk)  
    begin  
        if (rst) begin  
            s1 <= 1'b0;  
            s0 <= 1'b0;  
        end  
        else begin  
            s1 <= n1;  
            s0 <= n0;  
        end  
    end  
endmodule
```

more complex circuits :

 

opening a locked door by adding in a certain code

① encode states -

wait = 000

red1 = 010

green = 100

start = 001

blue = 011

red2 = 101

eg. → and then use 'parameter' to declare named constants
parameter st1 = 2'b00, st2 = 2'b01, st3 = 2'b10;

```

module pulse3 ( input s, r, g, b, a,
                input clk, rst,
                output u );

```

wait is a reserved keyword

```

parameter wait = 3'b000, start = 3'b001, red1 = 3'b010,
           blue = 3'b011, green = 3'b100, red2 = 3'b101;

```

```

reg [2:0] nst, st;

```

```

assign u = (st == red2);

```

→ returns 0 or 1

```

always @ (posedge clk) begin
    if (rst) st <= wait;
    else st <= nst;

```

```

end

```

```

always @ * begin

```

```

    nst = st;

```

← default; protects self-transition

```

    case (st)

```

```

        wait : if (s) nst = start;

```

```

        start : if (a)

```

```

            if (r & ~b & ~g) nst = red1;

```

```

            else nst = wait;

```

```

        red1 : if (a)

```

```

            if (b & ~r & ~g) nst = blue;

```

```

            else nst = wait;

```

```

        blue : if (a)

```

```

            if (g & ~r & ~b) nst = green;

```

```

            else nst = wait;

```

```
green : if(a)
        if (r&~q&~b) nst = red2;
        else nst = wait; ;
```

```
red2 : nst = wait
```


```
default : nst = wait ;
```

```
endcase
```

```
end
```

synchronous (pos..)

 - get a register
- \Rightarrow output is of a register
- $x = a + b$



combinational (*)

- no register (assignment is a wire)
- \Rightarrow output is of the adder

always