 



Shift Register

a shift register takes a single input and passes it through a chain of flip-flops. at each clock cycle, the input progresses one stage



internal signals are required to connect the registers and must be declared as reg type

```
module shiftreg(input clk, y,
                 output reg q);
```

```
    reg q1, q2, q3;
```

```
    always@(posedge clk)
    begin
```

```
        q1 <= y;
```

```
        q2 <= q1;
```

```
        q3 <= q2;
```

```
        q  <= q3;
```

```
    end
```

```
endmodule
```

old values

order
doesn't matter

another
option, →
next page

- using vectors ; shifting on command ; changing direction

```
module shiftreg (input clk, y, sh, rt,
                 output reg q-out);
```

```
    reg [3:1] q;
```

```
    always @ (posedge clk)
```

```
    begin ← if (sh) begin ← if (rt) begin ← q[4] <= y; q[3:0] <= q[4:1];
```

```
        q[1] <= y;
```

```
        → // q-out <= q[3];
```

```
        q[3:2] <= q[2:1];
```

} only 3 assignments
required

```
    assign q-out = rt ? q[0] : q[4];
```

```
endmodule
```

```
    reg [4:1] q;
```

```
    assign q-out = q[4];
```

```
    always @ (posedge clk)
```

```
    begin
```


```
        q[4:1] <= { q[3:1], y };
```

```
    end
```

can be
assigned
outside
always
block

• all outputs:

 - We might want to be able to access the whole word



```
module shiftreg4 (input clk, y, sh, rt,
                  output q_out,
                  output [4:0] q_word);

    reg [4:0] q;

    always@(posedge clk)
    begin
        if (sh) begin
            if (rt) begin
                q[4] <= y; q[3:0] <= q[4:1];
            end else begin
                q[0] <= y; q[4:1] <= q[3:0];
            end
        end
    end

    assign q_out = rt ? q[0] : q[4];
    assign q_word = q;
endmodule
```

parallel in/out \Rightarrow [a:b] type I/O \leftarrow many
serial in/out \Rightarrow wire type I/O \leftarrow just one

not v. imp

Serial Data Transfer

- one-bit at a time (sender)

\Downarrow

needs a parallel to serial converter (PISO)

\downarrow

serial to parallel converter (SIPO)

\downarrow

receiver

```
module piso4 (input clk, ld,  
              input [3:0] y,  
              output q_out);
```

```
  reg [3:0] q;  
  always @(posedge clk)  
  begin
```

```
    if (ld) q <= y;
```

```
    else begin
```

```
      q[0] <= y[0];
```

```
      q[3:1] <= q[2:0];
```


```
    end
```

```
  end
```

```
  assign q_out = q[3];
```

```
endmodule
```
 
```
module siipo4 (input clk, y,  
              output reg [3:0] q);  
  always @(posedge clk)  
  begin  
    q[0] <= y;  
    q[3:1] <= q[2:0];  
  end  
endmodule
```




parallel in - serial out \rightarrow serial in - parallel out

shift
converter

First-In-First-Out Buffer

same as shift registers, except each register is multibit
 
```
module fifo4 (input clk, input [3:0] y,  
              output reg [3:0] q);  
  
  reg [3:0] q1, q2, q3;  
  
  always@(posedge clk)  
  begin  
    q1 <= y;  
    q2 <= q1;  
    q3 <= q2;  
    q  <= q3;  
  end  
  
endmodule
```




Memories

- array of storage elements
- each register is a single storage element and has a unique address
- we should be able to select the register by its address and also read something out from the memories.

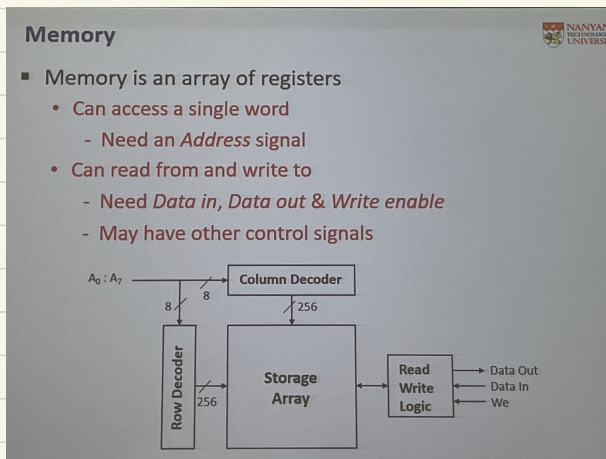8:57

- can access a single word (needs an address signal)



defined as an array of type reg

8-bit x 1024 memory:

reg [7:0] mem_array [0:1023];

memory
initialisation

■ A simple 8-bit x 1024 single port RAM module in Verilog

```
module dmem #(parameter WORD_SIZE = 8, ADD_SIZE = 10) (input clk, w
    input [WORD_SIZE-1:0] din, input [ADD_SIZE-1:0] add,
    output [WORD_SIZE-1:0] dout);
    → reg [WORD_SIZE-1:0] RAM [0:(1<<ADD_SIZE)-1]; // Define mem arra
    assign dout = RAM[add]; // Combinational read
    always @ (posedge clk)
        if (we) RAM[add] <= din; // Synchronous write
endmodule
```

→ shifts 1 by 10 places ⇒ 10000000
= $2^{10} = 1024$

$$y = \begin{matrix} & 2 & 1 & 0 \\ & 1 & 1 & 1 \\ \downarrow & \downarrow & \downarrow & \rightarrow \\ \downarrow & \downarrow & \downarrow & \rightarrow \\ \downarrow & \downarrow & \downarrow & \rightarrow \end{matrix}$$

$$q \leftarrow y \quad q = \begin{matrix} & 2 & 1 & 0 \\ & 1 & 1 & 1 \end{matrix}$$

$q[$