 



Combinational Circuits


- o/p is a f^n of present inputs
- $\Delta \text{input} \rightarrow \Delta \text{output}$ after a short propagation delay
- knowing current input \equiv predicting an output

Sequential Circuits


- introduce the idea of "state"
 - state of a circuit basically contains info generated in the past, and that info is used to determine what the output will be for the current input
 - hence, o/p depends on present and past inputs.
 - \therefore they have memory
- eg. pressing and then releasing a button, but wanting its effect to last until another button is pressed



1. Call button pressed - light turns on

 



2. Call button released - light stays on

 


3. Cancel button pressed - light turns off

• sequential logic

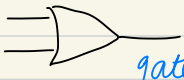
i)  can't store a value
gate

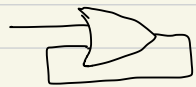ii)  can store a value, but it can't be replaced
feedback

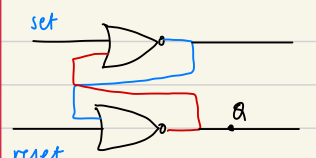
iii)  SR (set-reset) latch

SR	Q
1 0	1
0 1	0
1 1	fluctuating on & off
0 0	store

so when S & R are asserted / de-asserted at the same time, the output will oscillate, i.e. it will stabilize because one propagation is faster than the other, but it is impossible to know which one

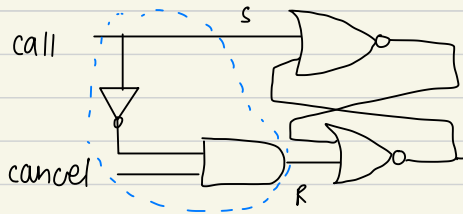 iv)  fixes above problem

but now there is a time delay b/w inverter & AND gate and so for a brief period the output does oscillate "call to R is longer than call to S"




gate/enabled SR latch

$E = 0 \rightarrow$ retains prev value
 $E = 1 \rightarrow$ changes

$Q \rightarrow$ o/p at current state
 $Q^+ \rightarrow$ o/p at next state


E	S	R	Q^+	F ⁿ
0	X	X	Q	store
1	0	0	Q	store
1	0	1	0	reset
1	1	0	1	set
1	1	1	?	undef.

 



removes chance
of invalid
inputs

transparent D latch

E	D	Q^+	f ⁿ
0	X	Q	store
1	0	0	reset
1	1	1	set

 


  vii) $\text{nor} \leftrightarrow \text{nand}$, $\text{or} \leftrightarrow \text{and}$



E.	D	Q+	fn
1	X	Q	store
0	0	0	trans-
0	1	1	parent

propagation delay (again)

 

give both values
if asked for one, then max value

the clock

- a signal that toggles between 0 & 1 at a fixed rate
- sequential components are connected to the clock
- oscillation of the clock gives MHz / GHz numbers for the chips
- period : $0 \rightarrow 1$ (ns)
freq = $\frac{1}{\text{period}}$ (GHz)
- we use only 1 clock in synchronously designed sequential circuits