 



- combinational circuits in VL
- sequential circuits (memory)
- state machines

Intro to Verilog

- hardware - description language
 - special languages with special constructs for describing hardware
 - can describe hardware at various levels of abstraction and hence enables hierarchical design
- V extension





HDL	Prog. Lang.
synthesize and optimise hardware primitives	compiled to primitive instructions to run on an existing piece of hardware


modules

- designs are broken-down into modules
- container a designer uses to encapsulate a unit of functionality
- and gate, adder, etc
- can contain instances of other modules
- good designs have sufficient hierarchy with modules containing instances of modules containing instances of modules

declaration

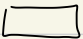eg1 `module <name> (port1, port2, port3);`
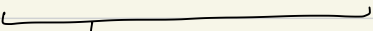
`endmodule`

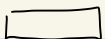 single wire, means of communication

eg2 `module <name> (input port1, port2,`

`output port3);`
`endmodule`

only assign & read

structural design in verilog

- describing a circuit by its internal structure
- 1. declare module
 2. introduce gates
 3. have wires
- primitives in verilog to model gates: and, nand, or, nor, not, xor, xnor

eg1 `and(y, a, b)` (`y, a, b` are signals)
 ↑ ↓
 o/p input ↳ either ports or wires

eg2 module w/ 2 input and.

```
module simple-AND (input in1, in2,  
                  output out);
```

```
    and(out, in1, in2);
```

```
endmodule
```

- * ports \equiv wires but o/p port can't be connected to an input port.
- * we wouldn't create a module for a gate that already exists as a primitive

- wires \rightarrow anchor pts to which you can connect logic
- internal wires can be declared in a module using wire keyword.

wire int_signal; \leftarrow 1-bit wire connects the gates

- Verilog module with gate level primitives
- and-or-inverter
- boolean exp: $out = ((a \cdot b) + (c \cdot d))'$

module andorinv (input a, b, c, d,
output out);

wire o1, o2; \leftarrow no need to declare 1-bit wires

and g1 (o1, a, b);
and g2 (o2, c, d);
nor g3 (out, o1, o2);

gate
identification

endmodule


half adder in verilog.

sum: $A \oplus B$ 2 i/p 2 o/u
carry: $A \cdot B$

```
module halfadder ( input a, b,  
                   output sum, carry );
```

```
    and g1 (carry, a, b);  
    xor g2 (sum, a, b);
```

```
endmodule
```

 

$$(A+D)' \cdot BCD' = Y$$

verilog rules

- order of instantiation doesn't matter
- case sensitive
- ;
- c-style comments (`//` or `/*...*/`)
- whitespace is ignored
- identifiers
 - letter / underscore as 1st char
 - letter / numbers / `$`
 - mustn't clash with keywords

module instantiation

$$s_2 = (A \oplus B) \oplus C$$

$$c_2 = AB + C(A \oplus B)$$

$$FA = HA + MA + OR$$

(input a, b,
output sum, cout)
if first
or second

module halfadder
xor g1 (sum, a, b);
and g2 (cout, a, b);
endmodule

module fulladder (input A, B, CIN, output SUM, COUNT);

or g1 (COUNT, w3, w2)
halfadder M2 (CIN, w1, SUM, w3)
halfadder M1 (A, B, w1, w2)

endmodule

alt: halfadder M1 (.a(A), .b(B), .sum(w1), .cout(w2));

unused ports should be left as : .b(), or ^{preferred} completely left out