


Limitations of D latches


propagation of a value through the latch is dependent on the time period of the clock and is hence hard to predict.

soln .


edge triggered flip-flops

logic: at each clock rising edge, each flip flop takes D input and gives Q output

 implemented: 2 step process using 2 oppositely enabled latches (master-slave)




has a delay

 


soln: use an active low version of the latch →

note: latch = level-sensitive (O/P changes when enable is 1)
 flip-flop = edge-triggered (+ve (0 → 1) or -ve (1 → 0))

↑
 assumed to be

 

latch

 


flip-flop

→ symbol: ▽
 on control input


- D flip flop : $Q = D$ at rising edge of C
- J-K flip flop : $Q = 1$ if J is asserted
 $Q = 0$ if K is asserted } at r.e of C
 Q toggles if $J \& K$ are asserted
- T flip-flop : Q toggles if $T = 1$ at r.e of C

Registers = multiple D flip-flops

stores multibit signals

 

"fundamental sequential component"

 

timing diagram :

